

# Simulating guitar distortion circuits by wave digital and Kirchhoff domain methods

David Yeh

Julius Smith

CCRMA / Stanford University



David Yeh

DAFx 2008  
TKK, Espoo, Finland

CCRMA

## Electronics are Musical Instruments

- Oscillators generate sound
- Amplifiers and filters modify sound
  - Dynamic Range Compressors (DRC), EQ, Reverb, Phaser/Flanger, Chorus, Voltage Controller Filter (VCF)
- Spectral palette for musicians



© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland

CCRMA

# “Virtual Analog”

- Field of music DSP
- Reproduce effects of analog circuits
  - Parametric linear filters
  - Nonlinear distortion
- Preservation of vintage musical effect circuits
- Flexibility – computer based studio





© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland

CCRMA
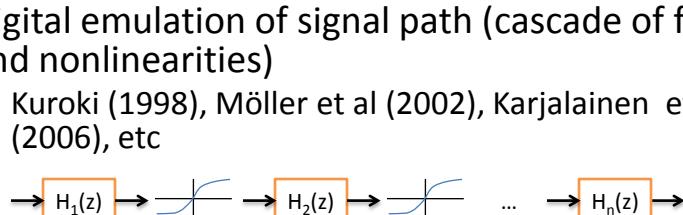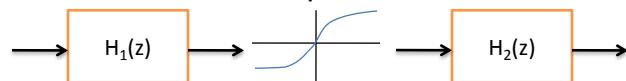
## Survey of existing methods

- Filters and static nonlinearity
  - Doidic et al. (1998), Schattschneider and Zölzer (1999), Abel and Berners (2005), Fernandez-Cid et al. (1999)
  - Tabulated / curve fit of parameter-coefficient map
- Digital emulation of signal path (cascade of filters and nonlinearities)
  - Kuroki (1998), Möller et al (2002), Karjalainen et al (2006), etc



© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland

CCRMA

## Numerical Simulation of ODE systems for Audio Effects



- Huovilainen (DAFx 2004, 2005) : Nonlinear Moog, modulation effects
- Yeh, et al. (DAFx 2007) : Diode clipper simulation
- Sarti and Tubaro (1999) : Nonlinear wave digital filters
- De Sanctis, et al. (DAFx 2003) : Automatic synthesis of WDFs
- Karjalainen and Pakarinen (2006) : WDF common cathode circuit
- Borin et al. (2000) : Eliminating delay free loops (K-method)
- Fontana, et al. (DAFx 2004) : Nonlinear filter networks

© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland
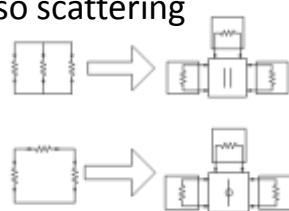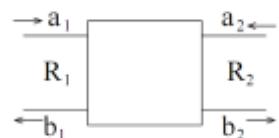
## Wave Digital Filter Principles



- Change of variable from voltage, current to waves  $a, b$ , and port impedance  $R$
- Circuit elements become scattering junctions
- Interconnection of elements are also scattering junctions (Adaptors)
  - N-port parallel and series junctions are  $O(N)$
  - Generic N-port scattering junction is  $O(N^2)$




© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland

## WDF Bright Switch

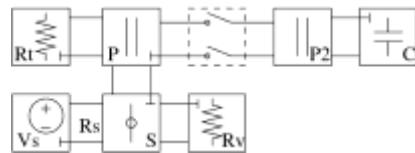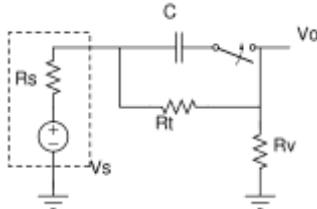


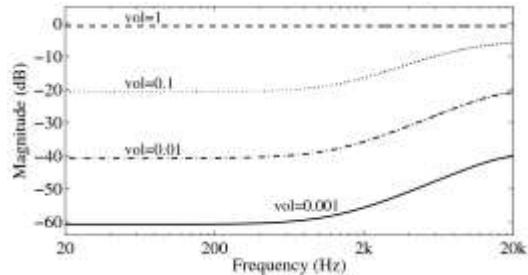
- Map circuit elements to WDF elements
- Parallel and series connections: efficient implementation
- Numerically robust and allows smooth parameter changes



© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland

## WDF Diode Clipper

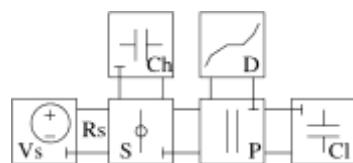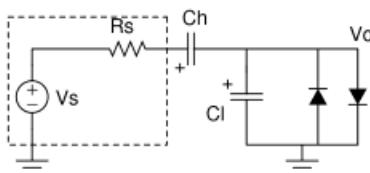


- Nonlinear element at top of WDF tree.
- Solve nonlinear equation for  $b = f(a)$

$$2I_s \sinh\left(\frac{a+b}{2V_t}\right) - \frac{a-b}{2R_p} = 0$$

© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland

## Multivariate state and nonlinearities

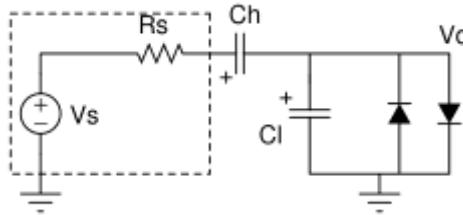

- Consider diode clipper with high pass capacitor
- Seek a systematic way to solve nonlinear ODE

© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland


## SSMN – State Space with Memoryless Nonlinearity (K-Method)

- State  $\mathbf{x}$  is capacitor voltages, inductor currents
- Inputs  $\mathbf{u}$  are independent sources
- Nonlinear vector  $\mathbf{i}$ : nonlinear voltage controlled current sources – diodes, transistors
- Vector of controlling voltages  $\mathbf{v}$
- Discretize system time-derivative by integration formula (BE) and solve for  $\mathbf{x}[n]$

$$\dot{\mathbf{x}} = \mathbf{Ax} + \mathbf{Bu} + \mathbf{Ci}$$

$$\mathbf{i} = \mathbf{f}(\mathbf{v})$$
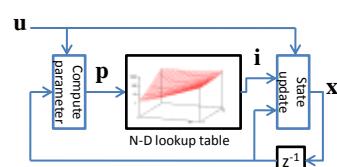
$$\mathbf{v} = \mathbf{Dx} + \mathbf{Eu} + \mathbf{Fi}$$




- Solution derives a memoryless nonlinearity
- Parameter  $\mathbf{p}$  is linear combination of  $\mathbf{u}$  and  $\mathbf{x}$

© 2008 David Yeh



DAFx 2008  
TKK, Espoo, Finland

## Diode clipper revisited

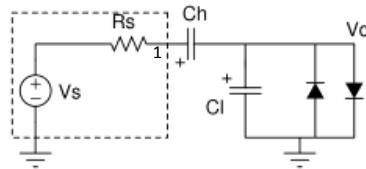

$$\mathbf{x} = \begin{bmatrix} V_{Ch} \\ V_{Cl} \end{bmatrix} \quad \mathbf{u} = [V_s]$$
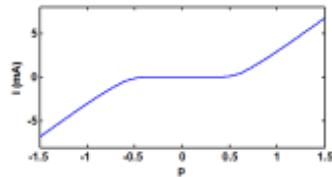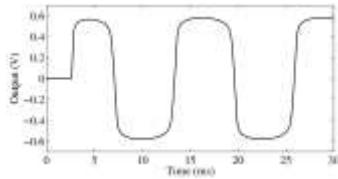
$$\mathbf{i} = \begin{bmatrix} I_s(\exp(V_o/V_t) - 1) \\ -I_s(\exp(-V_o/V_t) - 1) \end{bmatrix}$$



- Solution to implicit nonlinear mapping from  $\mathbf{p}$   
->  $\mathbf{i}$  can be tabulated

© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland


## Comparison of WDF and SSMN Diode Clippers

- Results are identical in MATLAB
- Assuming nonlinearity in algorithm is precomputed:
- WDF
  - Parallel/series scattering junctions
    - 4 multiplies
    - 8 adds
- SSMN
  - Matrix-vector multiplies
    - 13 multiplies
    - 12 adds

© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland


## SSMN common-emitter amplifier

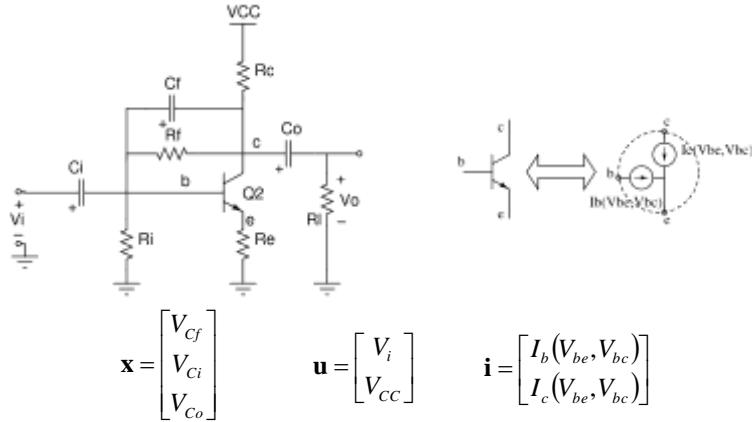



© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland

## Common-emitter results

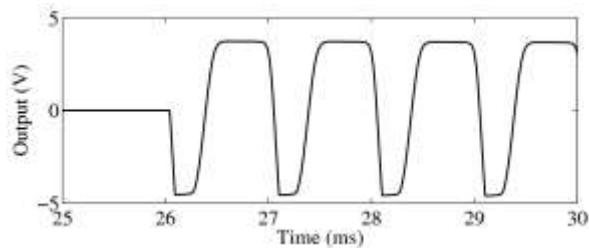


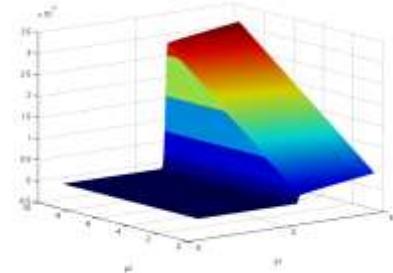
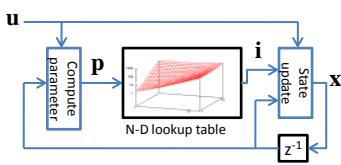
- 2D nonlinear mapping from parameter vector  $\mathbf{p}$  to device currents  $\mathbf{i}$



© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland

## SSMN common-cathode tube preamp

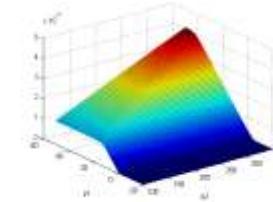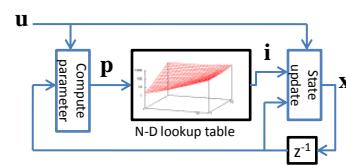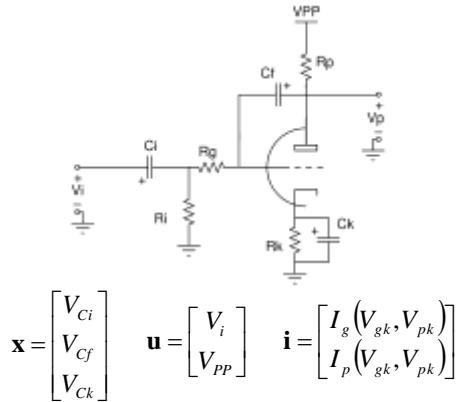


- 2D nonlinear mapping from parameter vector  $\mathbf{p}$  to device currents  $\mathbf{i}$

© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland
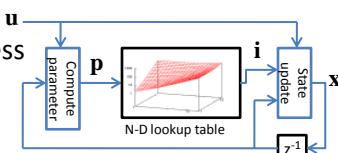
## Numerical methods for distortion effects extend prior work in musical acoustics.

- Explored application of WDF and SSMN to guitar distortion circuits
- WDF
  - Efficient and robust for special cases
  - Hard to apply in general situation: subject of ongoing research
- SSMN
  - Procedure to map circuits to SSMN formulation
  - Matrix-vector operations can be fast
  - Resulting static nonlinearity depends on sampling rate
- Numerical approximation of ODE yields recursive filter with static nonlinearity
  - Resulting nonlinearity is still memoryless
  - Memory is entirely in state vector



© 2008 David Yeh

DAFx 2008  
TKK, Espoo, Finland

